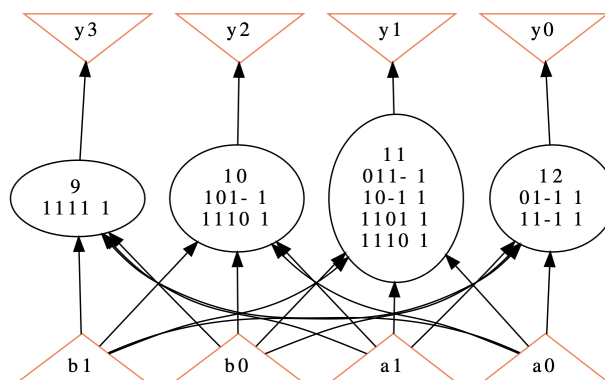


r12921045 電機碩一劉虹伶

(a) create a BLIF file named "mul.blif"




4. convert to AIG (command "strash")
5. visualize the AIG (command "show")

```
abc 02> strash
abc 03> show
```


Network structure visualized by ABC  
Benchmark "mul". Time was Thu Sep 14 14:22:58 2023.

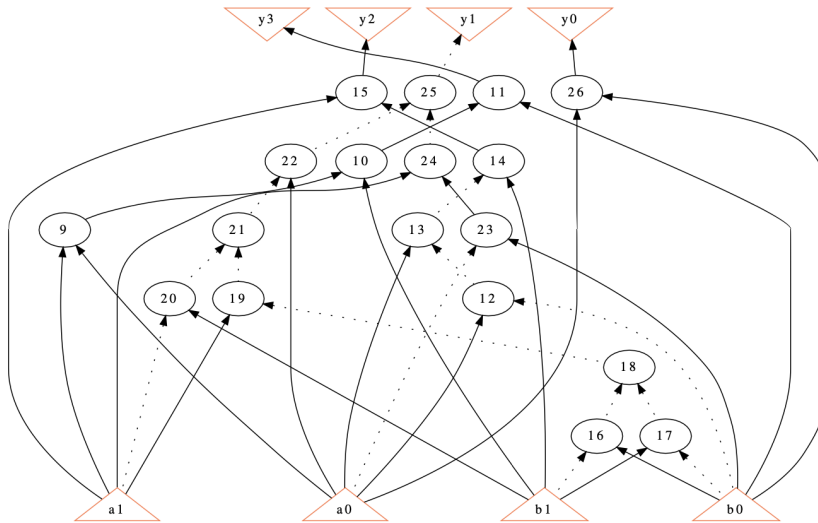The network contains 18 logic nodes and 0 latches.



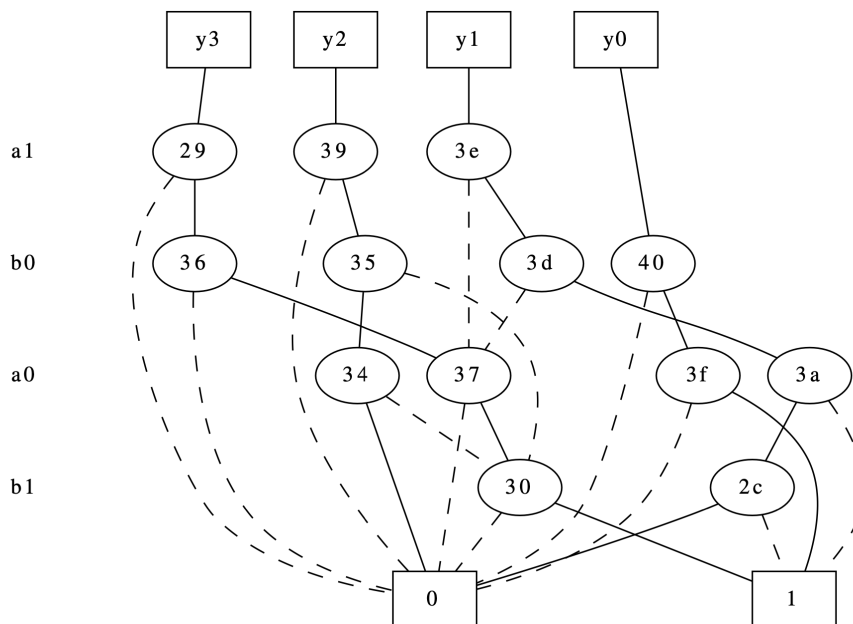6. convert to BDD (command "collapse")
7. visualize the BDD

```
abc 03> collapse
abc 04> show_bdd -g
```



### 3 [ABC Boolean Function Representations]

(a) Compare the following differences with the two-bit unsigned multiplier example. Screenshot the results and briefly describe your findings in your report.

1. logic network in AIG (by command "aig") vs. structurally hashed AIG (by command "strash" )

	aig	strash
result		
finding	<p>Converts local functions of the nodes to AIGs.</p> <p>It's still the same as the original one.</p>	<p>Transforms the current network into an AIG by one-level structural hashing. The resulting AIG is a logic network composed of two-input AND gates and inverters represented as complemented attributes on the edges.</p>

2. logic network in BDD (by command "bdd") vs. collapsed BDD (by command "collapse")

	bdd (show_bdd -g)	collapse (show_bdd -g)
result		
finding	<p>Converts local functions of the nodes to BDDs.</p> <p>- It's still the same as the collapsed one.</p>	<p>Recursively composes the fanin nodes into the fanout nodes resulting in a network, in which each CO is produced by a node, whose fanins are CIs. Collapsing is performed by building global functions using BDDs and is, therefore, limited to relatively small circuits. After collapsing, the node functions are represented using BDDs.</p>


(b) Given a structurally hashed AIG, find a sequence of ABC commands to convert it to a logic network with node function expressed in sum-of-products (SOP). Use the two-bit unsigned multiplier example to test your command sequence, screenshot the results, and put them in your report.

ANS: command "logic"

```
abc 01> read mul.blif
abc 02> strash
abc 03> logic
```

Network structure visualized by ABC  
Benchmark "mul". Time was Thu Sep 14 17:10:13 2023.

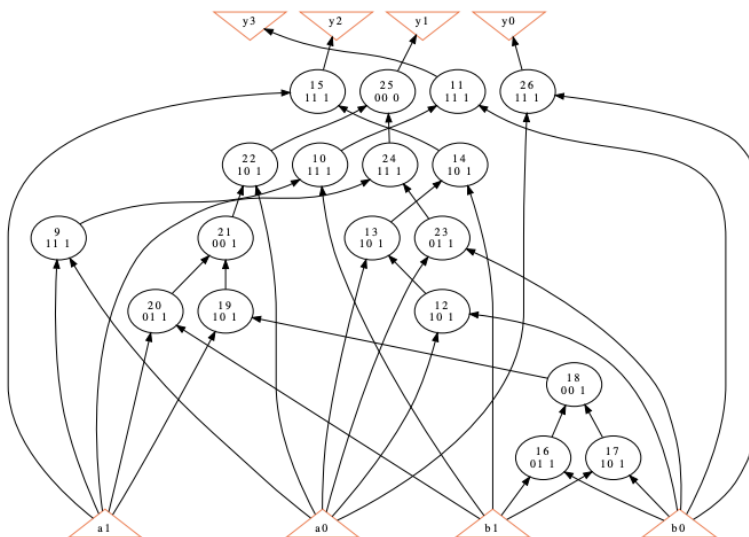The network contains 18 logic nodes and 0 latches.



## Reference

<https://people.eecs.berkeley.edu/~alanmi/abc/>